

Final Project - Two Stage OP



Design Flow


- Reference:
 - P. E. Allen and D. R. Holberg, "CMOS Analog Circuit Design," 2012
 - Chapter 6.3

6.3 Design of the Two-Stage Op Amp

- You can finish the two stage OP Amp step by step



Schematic

 

Spec

	SPEC	Unit
VDD	1.8	V
C_L	1	pF
DC Gain	> 70	dB
GBW	> 5	MHz
Phase Margin	≥ 60	degree
Slew Rate	> 5	V/ μ s
Power Dissipation	< 50	μ W
FoM	$\frac{A_v(dB) \times GBW(MHz)}{P(mW)}$	The larger the better



報告要求


- 報告中須包含設計流程，模擬結果須一併附上自己的觀察看法
- 報告中須包含performance table，如下

	SPEC	This Work	Unit
VDD	1.8	1.8	V
C_L	1	1	pF
DC Gain	> 70	89.9	dB
GBW	> 5	8.76	MHz
Phase Margin	≥ 60	64	degree
Slew Rate	> 5	6.98	V/ μ s
Power Dissipation	< 50	34.92	μ W
FoM	$\frac{A_v(dB) \times GBW(MHz)}{P(\mu W)}$	22.55	The larger the better





Appendix – 建立symbol

- Create – cellview – from cellview

 


Appendix – 建立symbol

- 按ok
- 依照個人需求擺放PIN的位置

  


Appendix – 建立symbol

- 完成symbol，可直接關掉此視窗

 


Appendix – testbench

 - 新建一個schematic
- 用i叫出剛剛產生的symbol，接上各電位後，後續模擬步驟與先前作業相同(ADEL.....)





Example – AC Response

 

Example – Slew Rate

- 接成unit gain buffer
- 測量在rise時，vout的斜率

  

Example – Slew Rate

